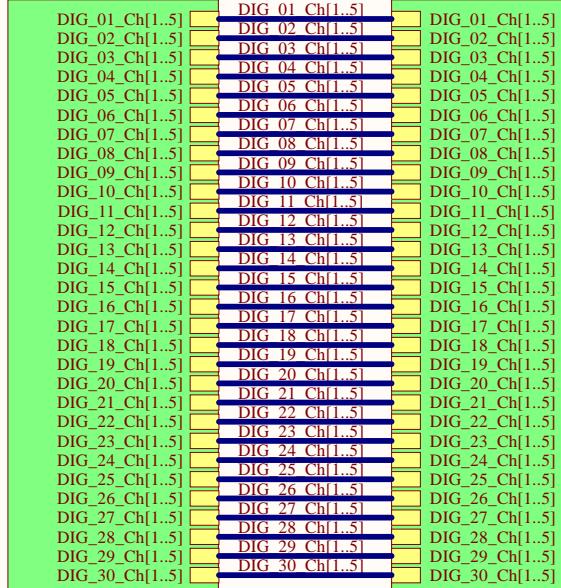
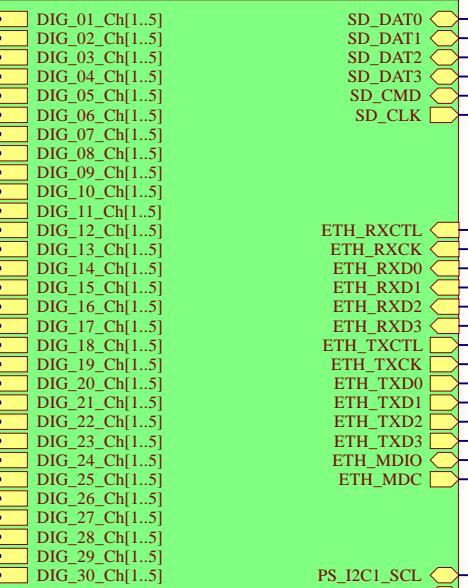
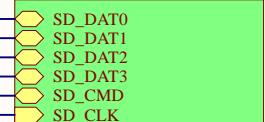
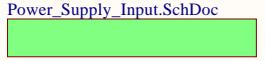
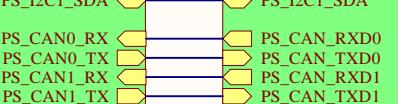
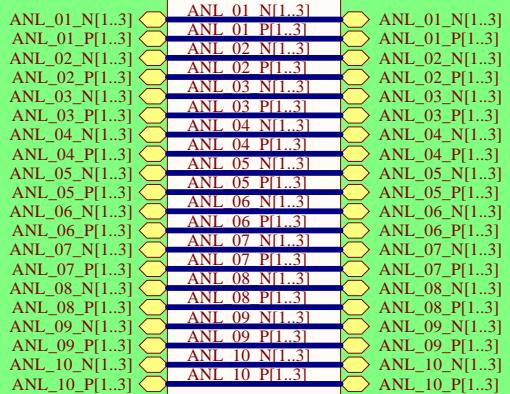
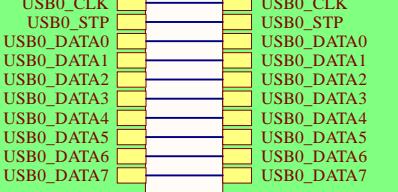
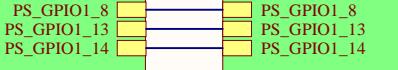
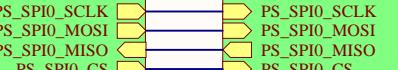
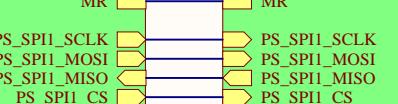
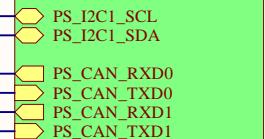


U_Signal_Distribution
Signal_Distribution.SchDoc

U_Board2Board
Board2Board.SchDoc

U_SD_Card
SD_Card.SchDoc

U_Power_Supply_Input
Power_Supply_Input.SchDoc

U_Block_Diagram
Block_Diagram.SchDoc


A

A


U_XMOD
XMOD.SchDoc


design information, revision number, ...


 Serial 1
 Serial
 Serialnumber 6.3 x 6.3mm


mounting holes for M3 screws



Title CarrierBoard_TopSheet.SchDoc		Technische Hochschule Nürnberg Georg Simon Ohm
Size: A4		Wassertorstr. 10
Revision: 3v00		90489 Nürnberg
GERMANY		
Date: 17.06.2020	Time: 23:24:31	Sheet 1 of 22
Project: UltraZOHM_CarrierBoard.PnjPcb	Author: Andreas Geiger	



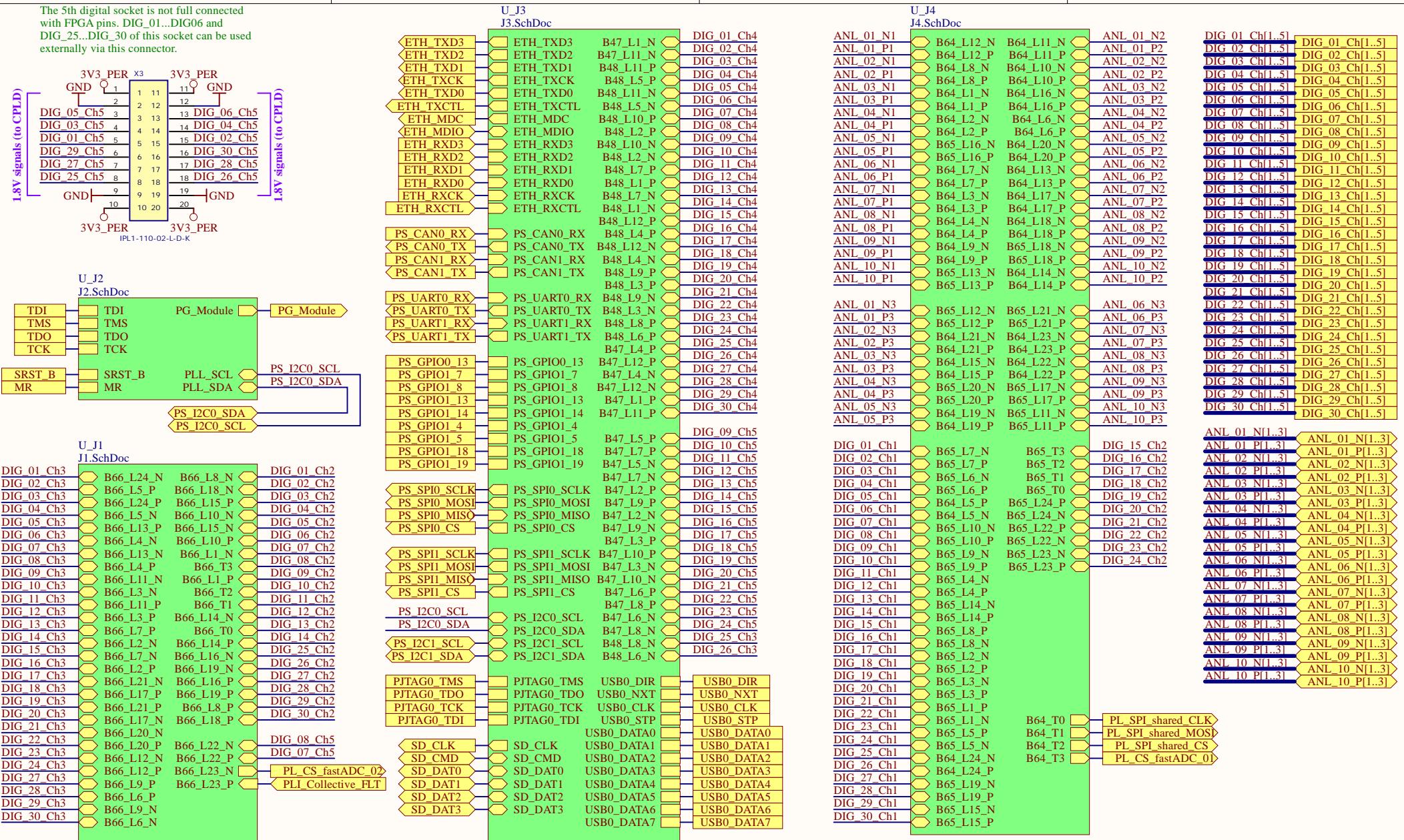

Title Board2Board.SchDoc Technische Hochschule Nürnberg Georg Simon Ohm
 Wassertorstr. 10
 90489 Nürnberg
 GERMANY

Size: A4 Revision: 3v00

Date: 17.06.2020 Time: 23:24:31 Sheet 2 of 22 Author: Andreas Geiger

Project: UltraZOhm CarrierBoard.PriPeb



A

B

C


D

A

B


C

D

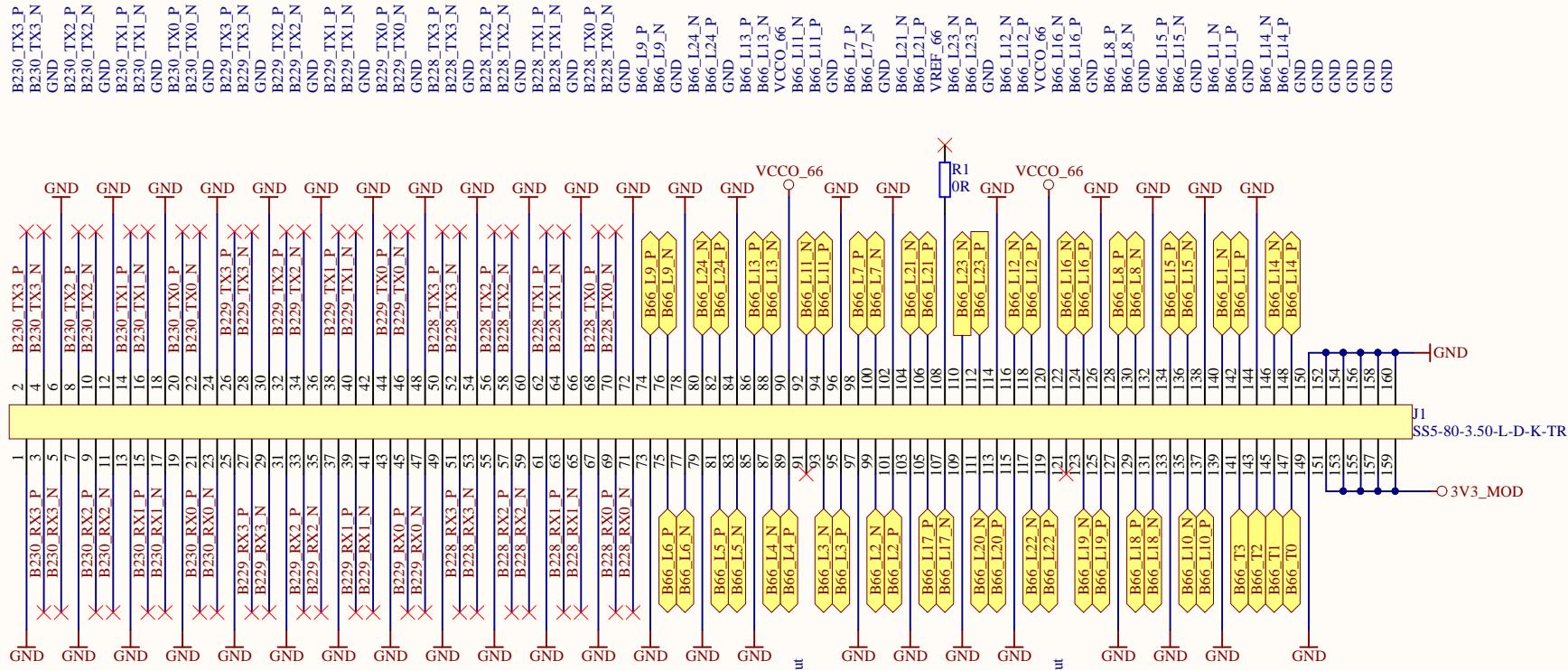

Title	J1.SchDoc	Technische Hochschule Nürnberg Georg Simon Ohm Wassertorstr. 10 90489 Nürnberg GERMANY
Size:	A4	Revision: 3v00
Date:	17.06.2020	Time: 23:43:32



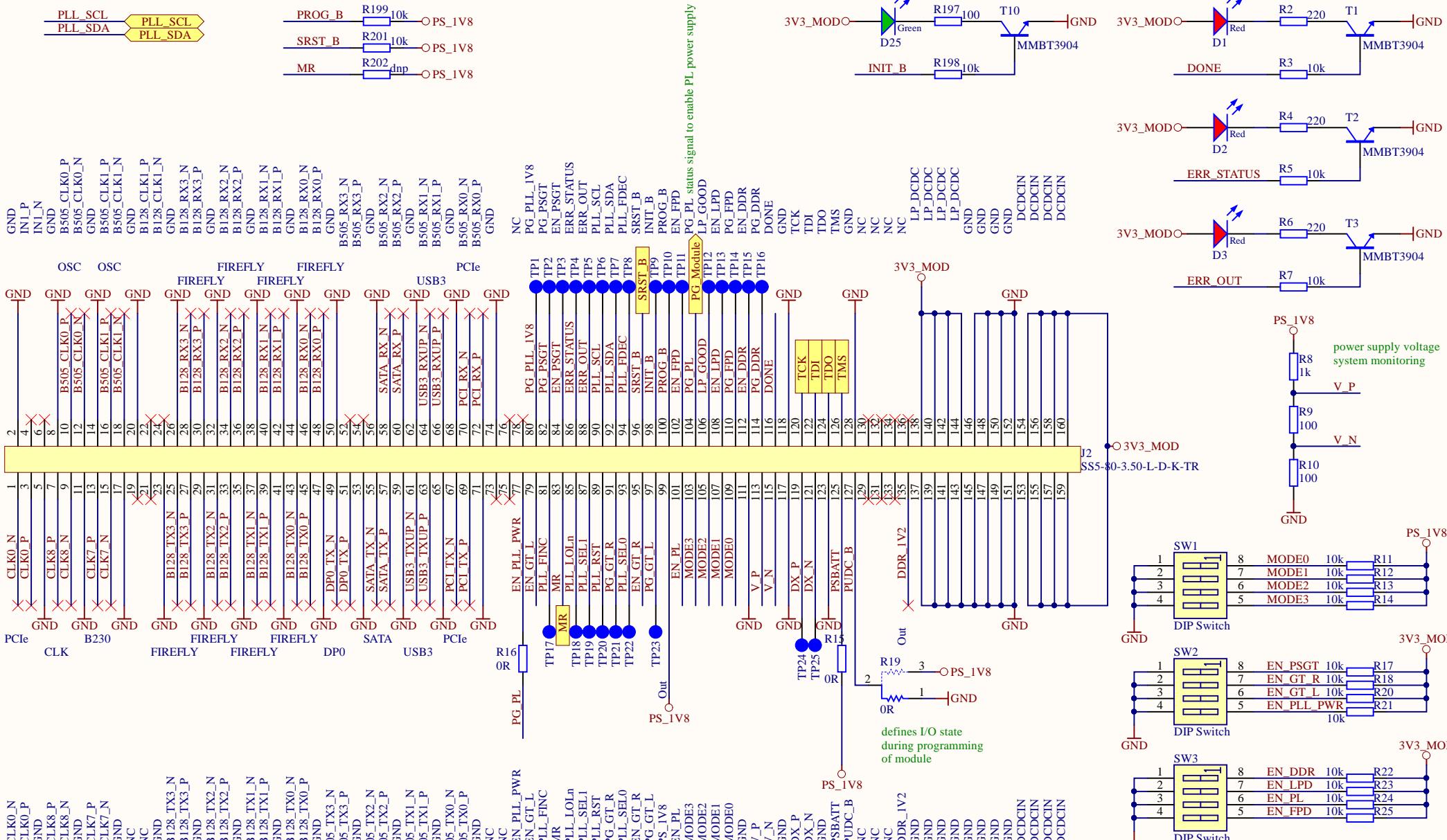

GND

Title J2.SchDoc	Technische Hochschule Nürnberg Georg Simon Ohm Wassertorstr. 10 90489 Nürnberg GERMANY	
Size: A4	Revision: 3v00	
Date: 17.06.2020	Time: 23:24:32	Sheet 4 of 22
Project: UltraZOhn CarrierBoard.PriPcb		Author: Andreas Geiger

A

B

C


D

A

B

C


D

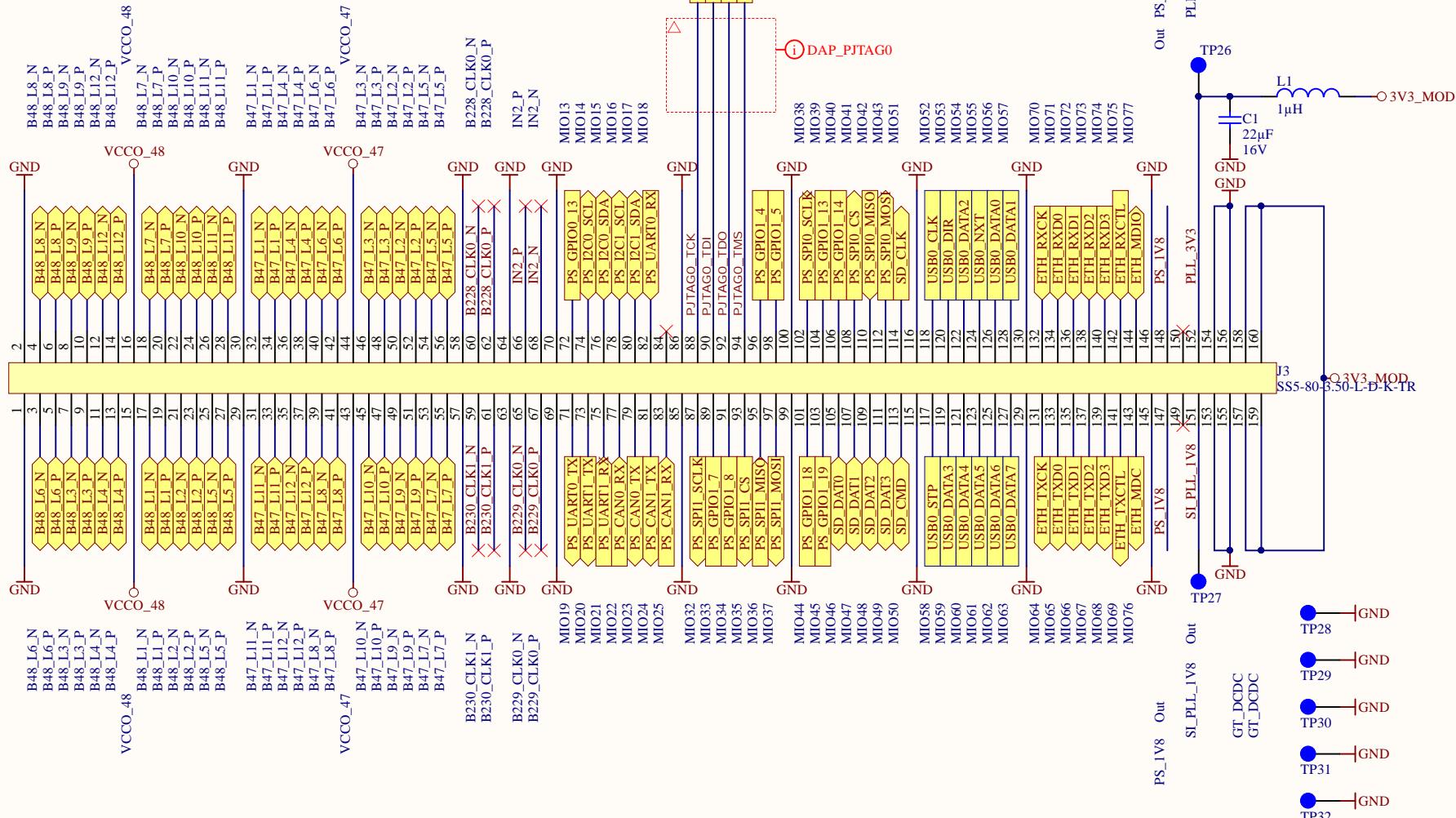

Title J3.SchDoc		Technische Hochschule Nürnberg Georg Simon Ohm Wasserstr. 10 90489 Nürnberg GERMANY	
Size: A4	Revision: 3v00		
Date: 17.06.2020	Time: 23:24:32	Sheet 5 of 22	Author: Andreas Geiger
Project: UltraZOHM_CarrierBoard.PnjPcb			







1

1








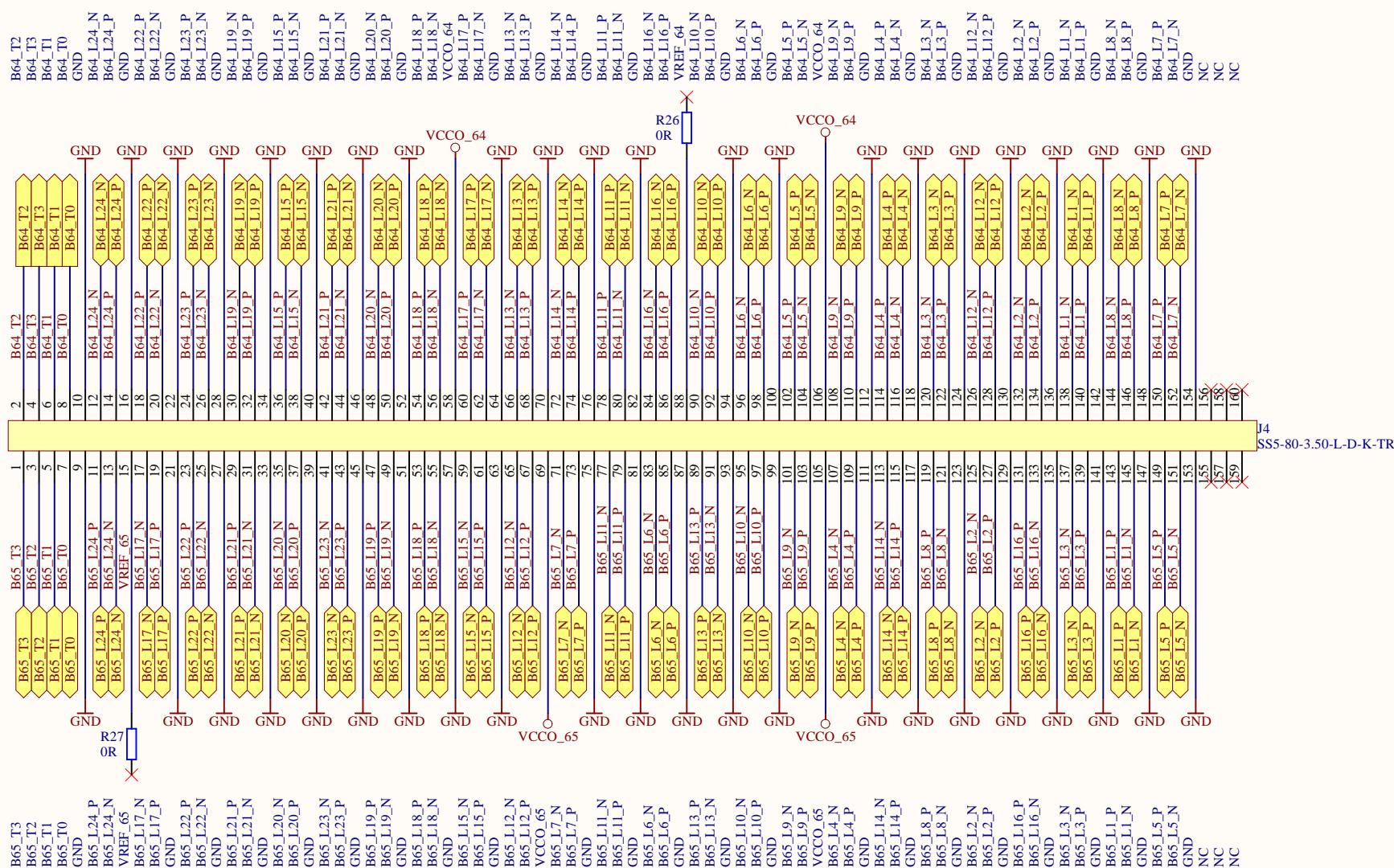


Title J4.SchDoc		<i>Technische Hochschule Nürnberg Georg Simon Ohm Wassertorstr. 10 90489 Nürnberg GERMANY</i>	
Size: A4	Revision: 3v00		
Date: 17.06.2020	Time: 23:24:32	Sheet 6 of 22	Author: Andreas Geiger
Project: UltraZOhm_CarrierBoard.PjrPcb			

A

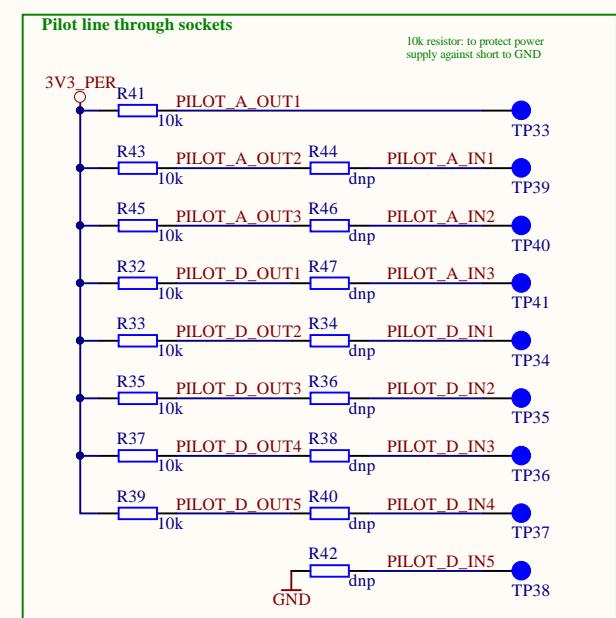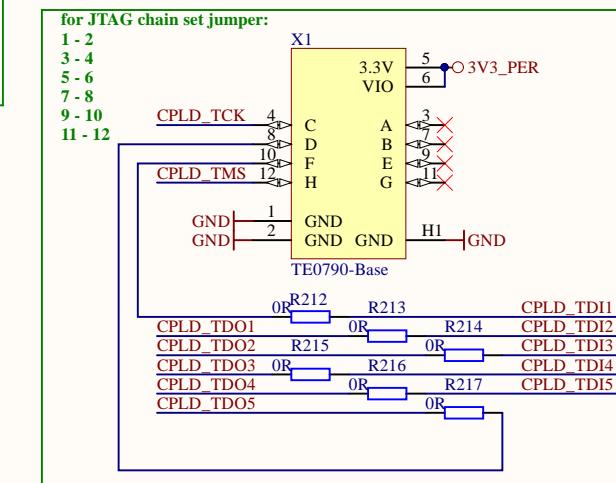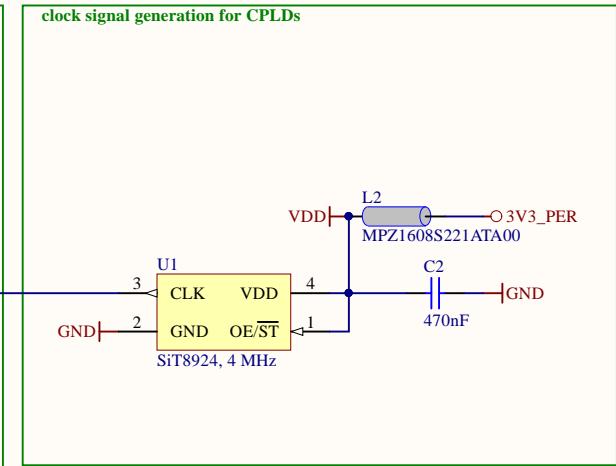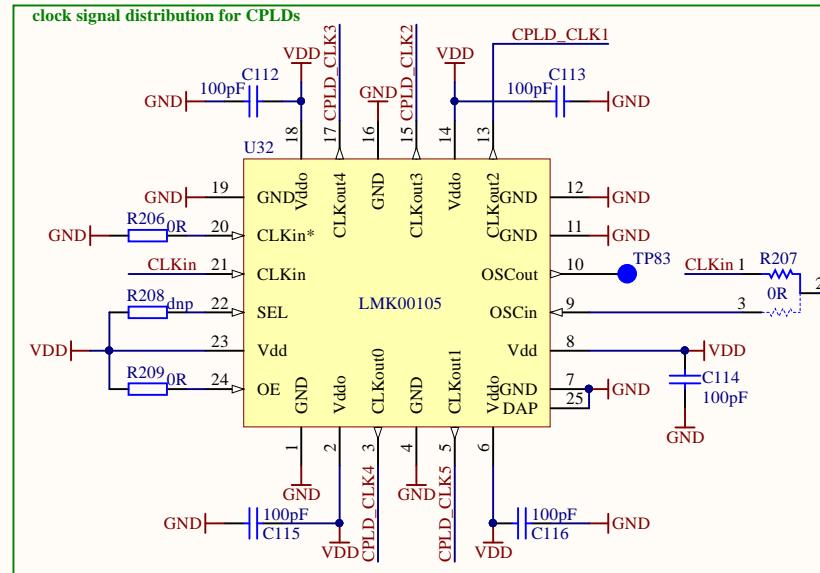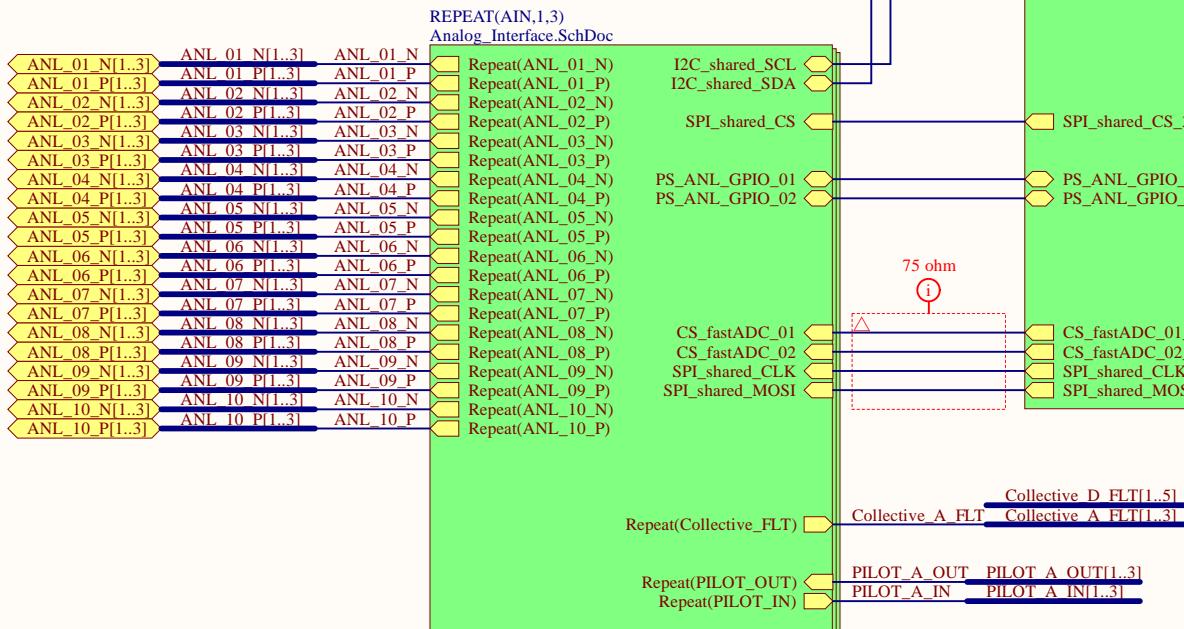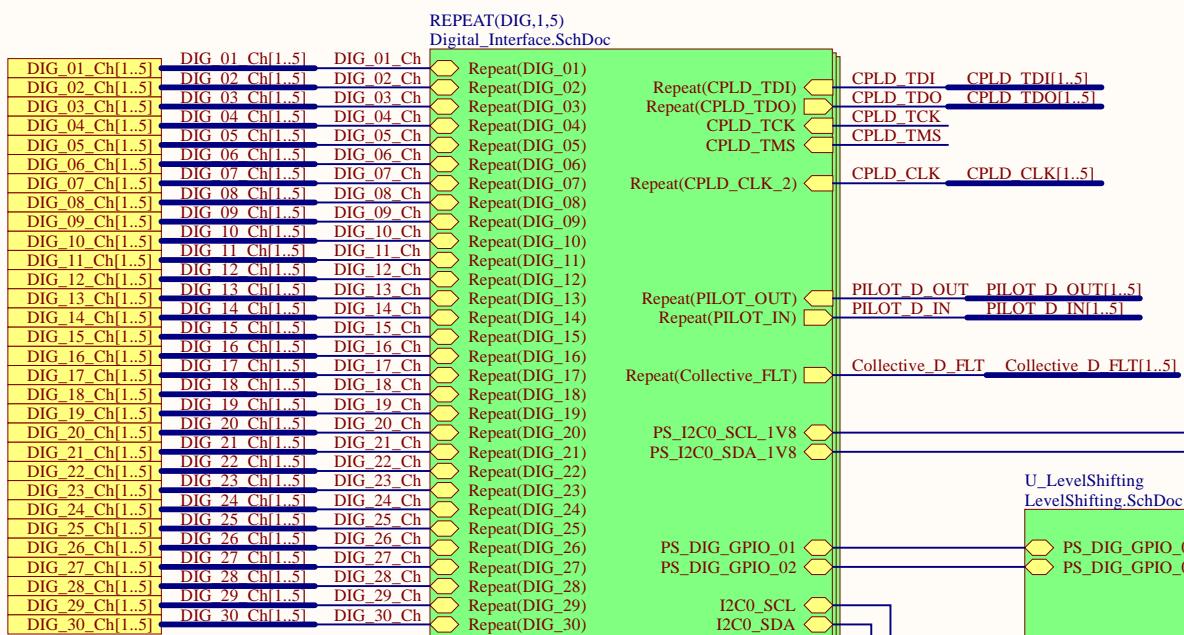

Title: Signal_Distribution.SchDoc	Technische Hochschule Nürnberg Georg Simon Ohm Wassertorstr. 10 90489 Nürnberg GERMANY	
Size: B	Revision: 3v00	
Date: 17.06.2020	Time: 23:43:32	Sheet 7 of 22
Project: UltraZOHM_CarrierBoard.PnjPcb	Author: Andreas Geiger	

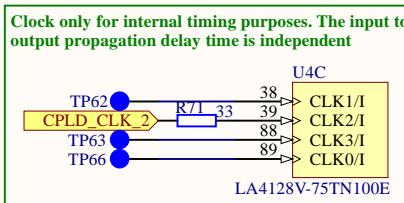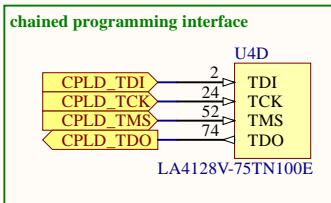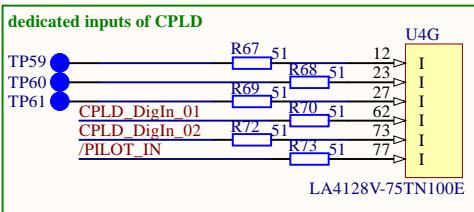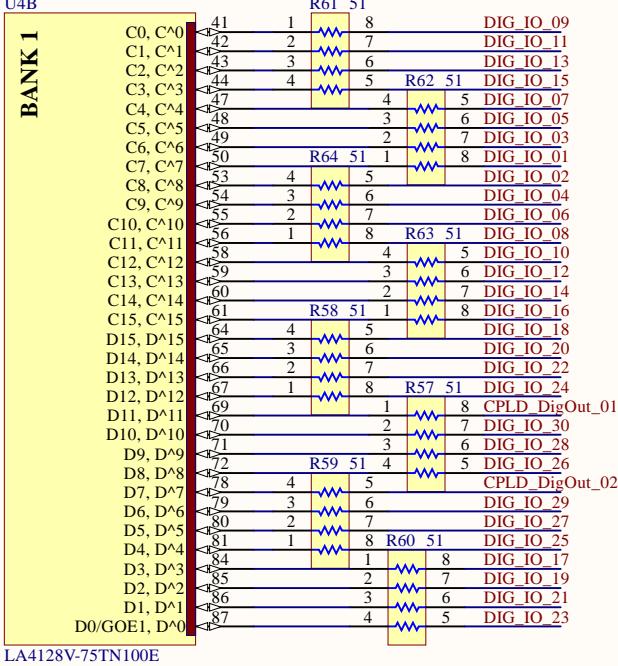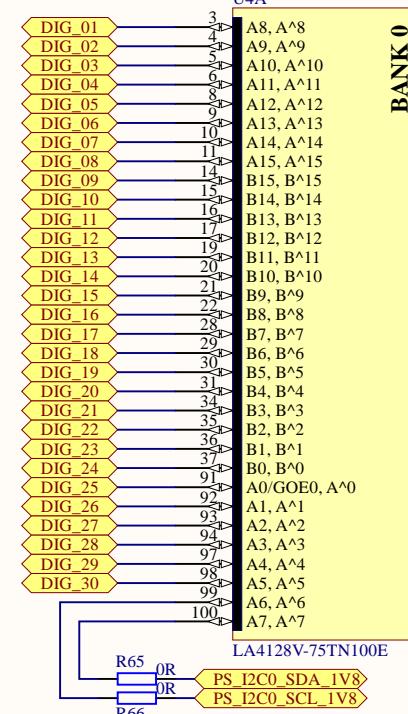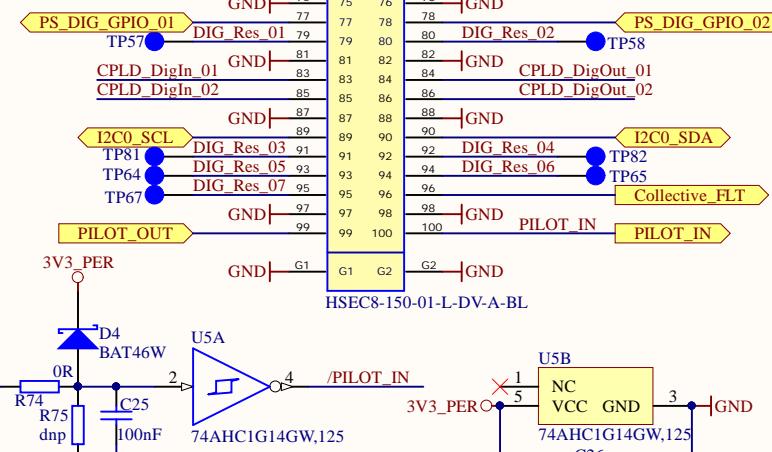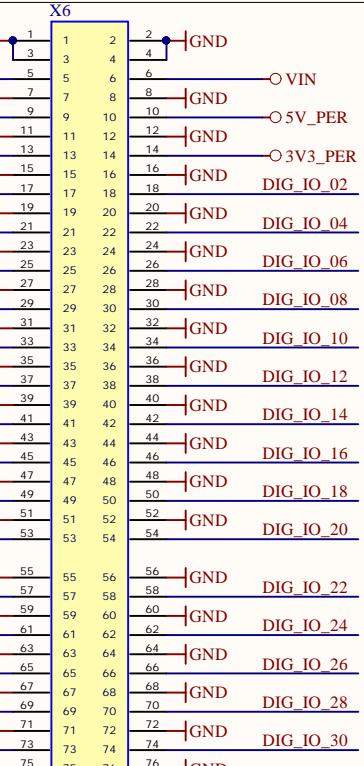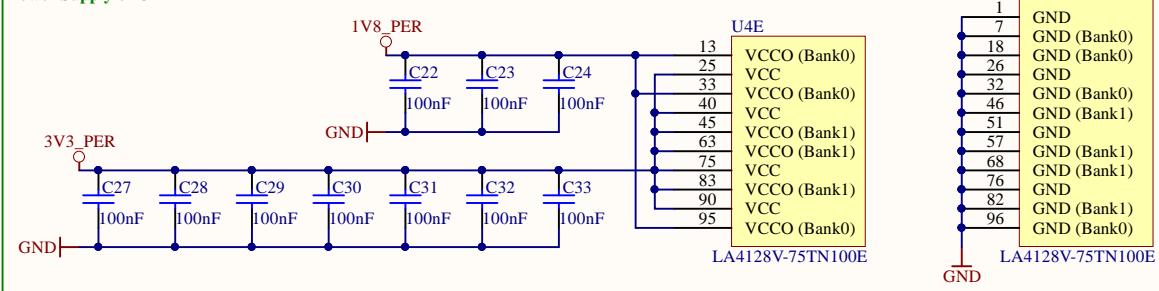BANK 0 @ 1.8V**BANK 1 @ 3.3V****Power Supply of CPLD**

Title: Digital_Interface.SchDoc	Technische Hochschule Nürnberg Georg Simon Ohm Wassertorstr. 10 90489 Nürnberg GERMANY
Size: A4	Revision: 3v00
Date: 17.06.2020	Time: 23:24:33
Project: UltraZOHM_CarrierBoard.PrtPcb	Sheet 8 of 22 Author: Andreas Geiger



A

B

6


B

1

1

1


1

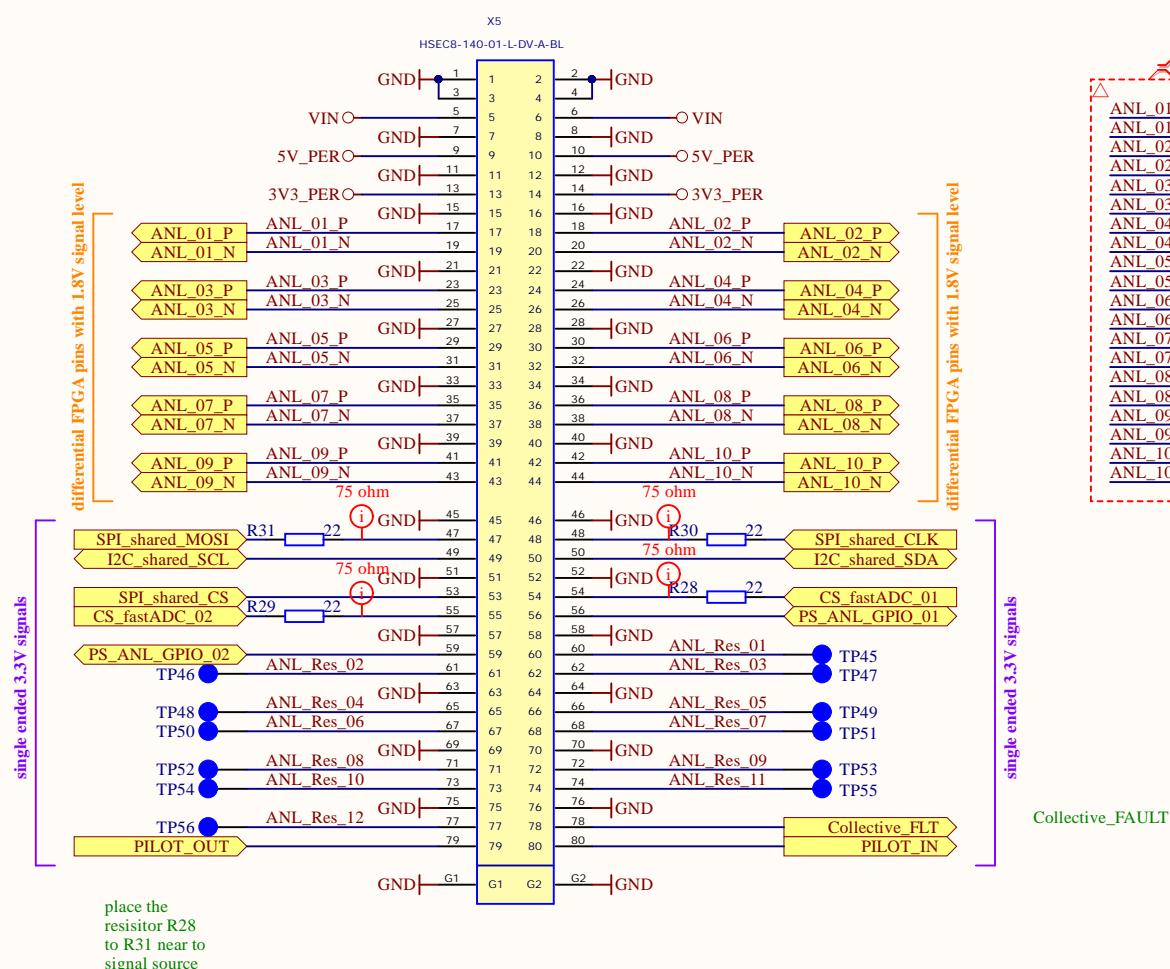


Note: The net labels do not float but altium says that they do because the nets are not connected to a pin

Title: Analog_Interface.SchDoc	<i>Technische Hochschule Nürnberg Georg Simon Ohm Wasserkunstr. 10 90489 Nürnberg GERMANY</i>	
Size: A4	Revision: 3v00	
Date: 17.06.2020	Time: 23:24:33	Sheet 9 of 22 Author: Andreas Geiger
Project: UltraZOhm CarrierBoard.PriPcb		

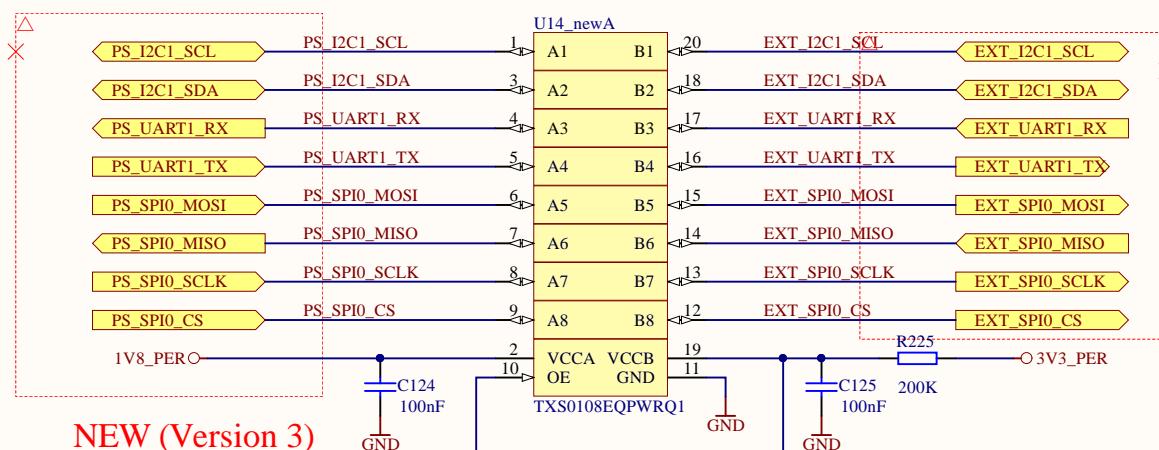Bidirectional Level Shifting 1.8V to 3.3V



OLD (Version 2)

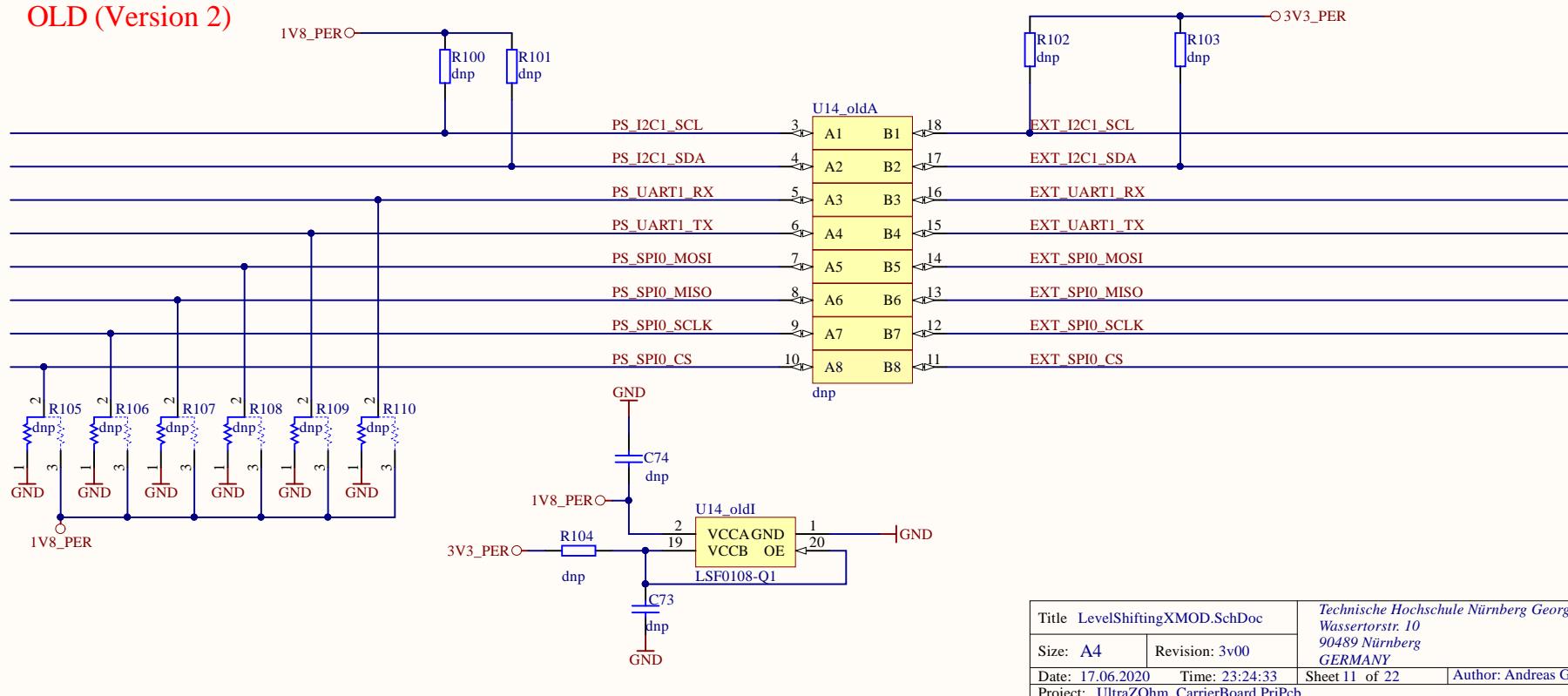


Note: In the layout
U14_old and U14_new do
not have a alphabetical
suffix it is only called
U14_old and U14_new.

Either the old or the new
level shifter must be
assembled but not both


Title: LevelShiftingXMOD.SchDoc	Technische Hochschule Nürnberg Georg Simon Ohm Wassertorstr. 10 90489 Nürnberg GERMANY	
Size: A4	Revision: 3v00	
Date: 17.06.2020	Time: 23:24:33	Sheet 11 of 22
Project: UltraZOHM_CarrierBoard.PnjPcb	Author: Andreas Geiger	



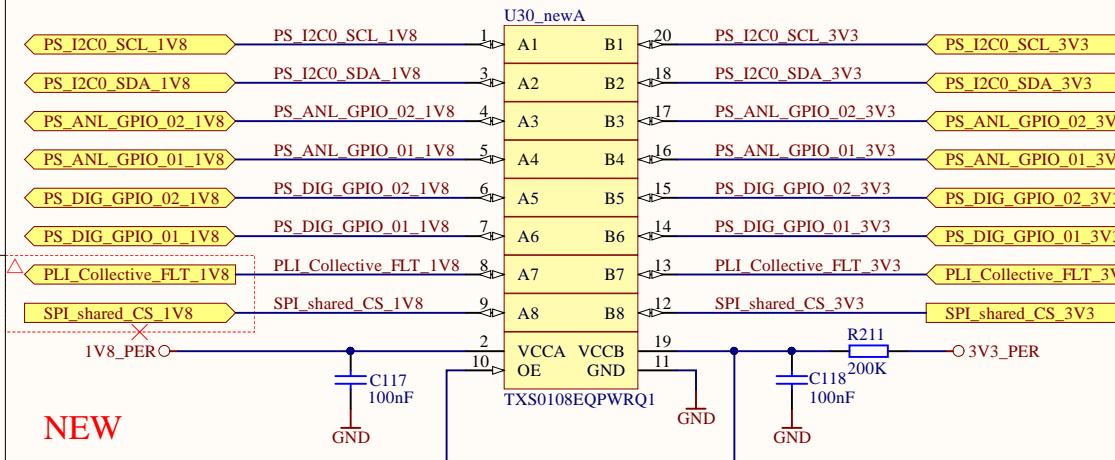
Bidirectional Level Shifting 1.8V to 3.3V



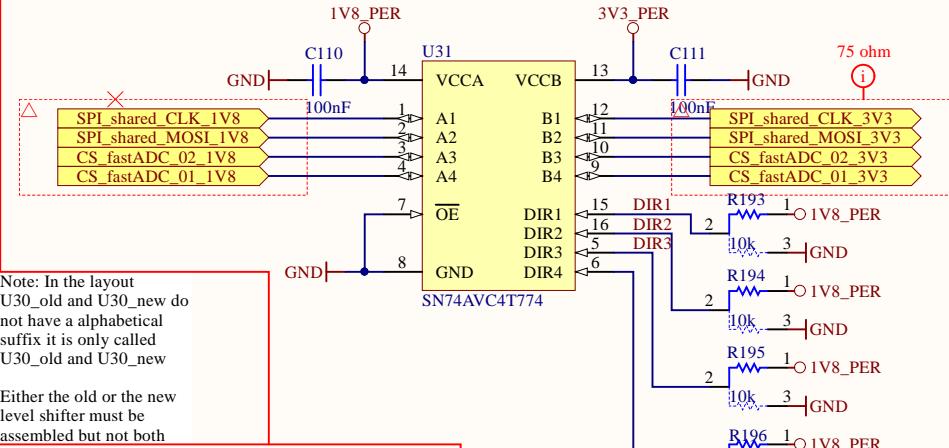
Unidirectional level Shifting 1.8V to 3.3V




OLD

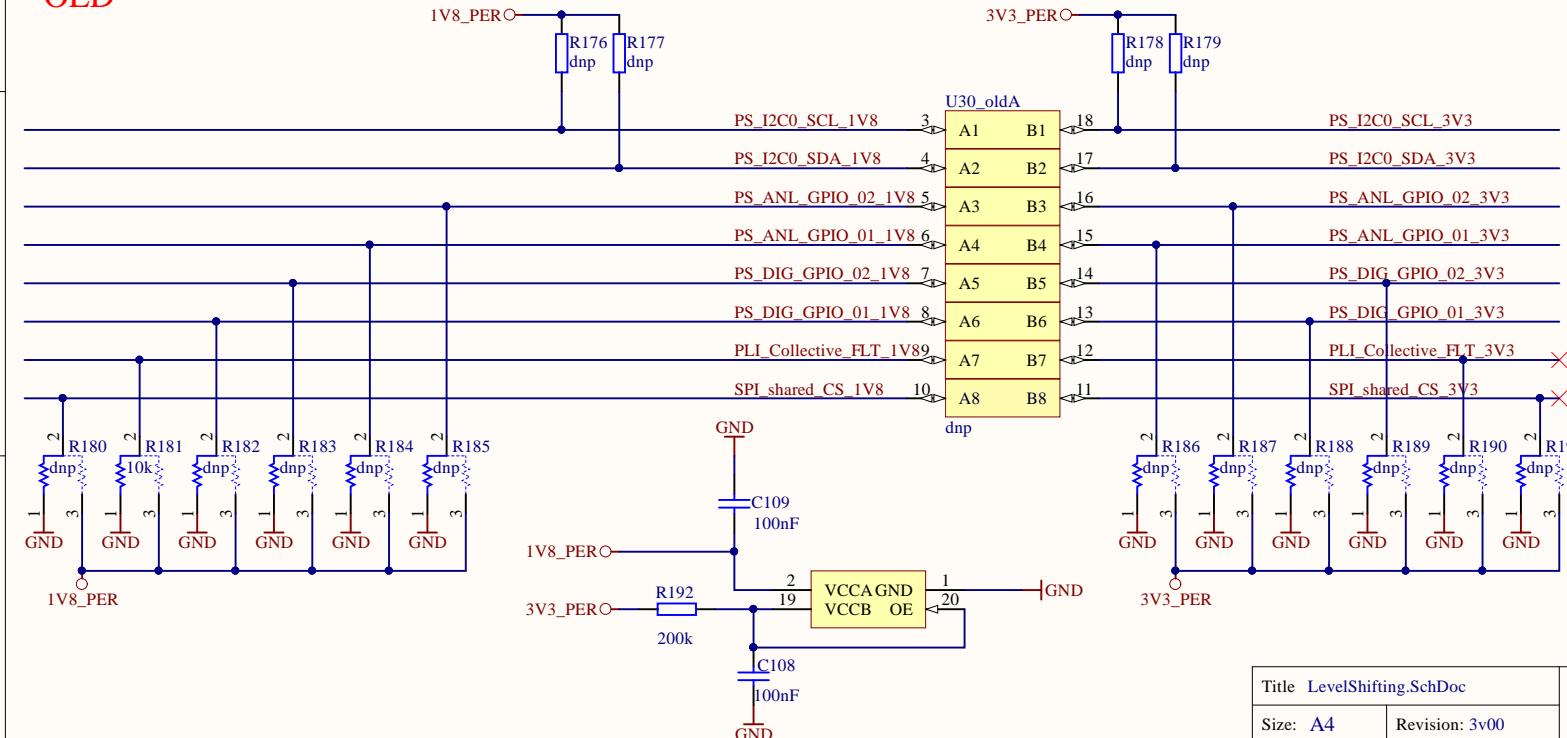

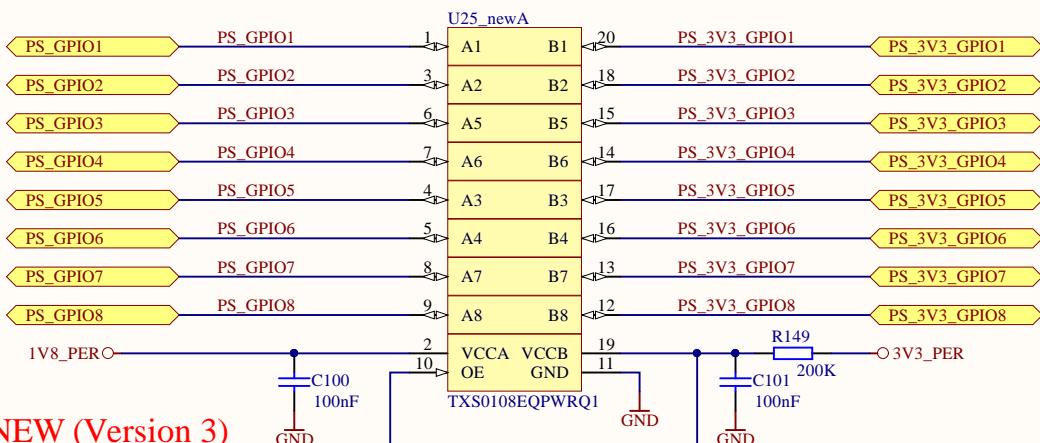Bidirectional Level Shifting 1.8V to 3.3V



OLD (Version 2)

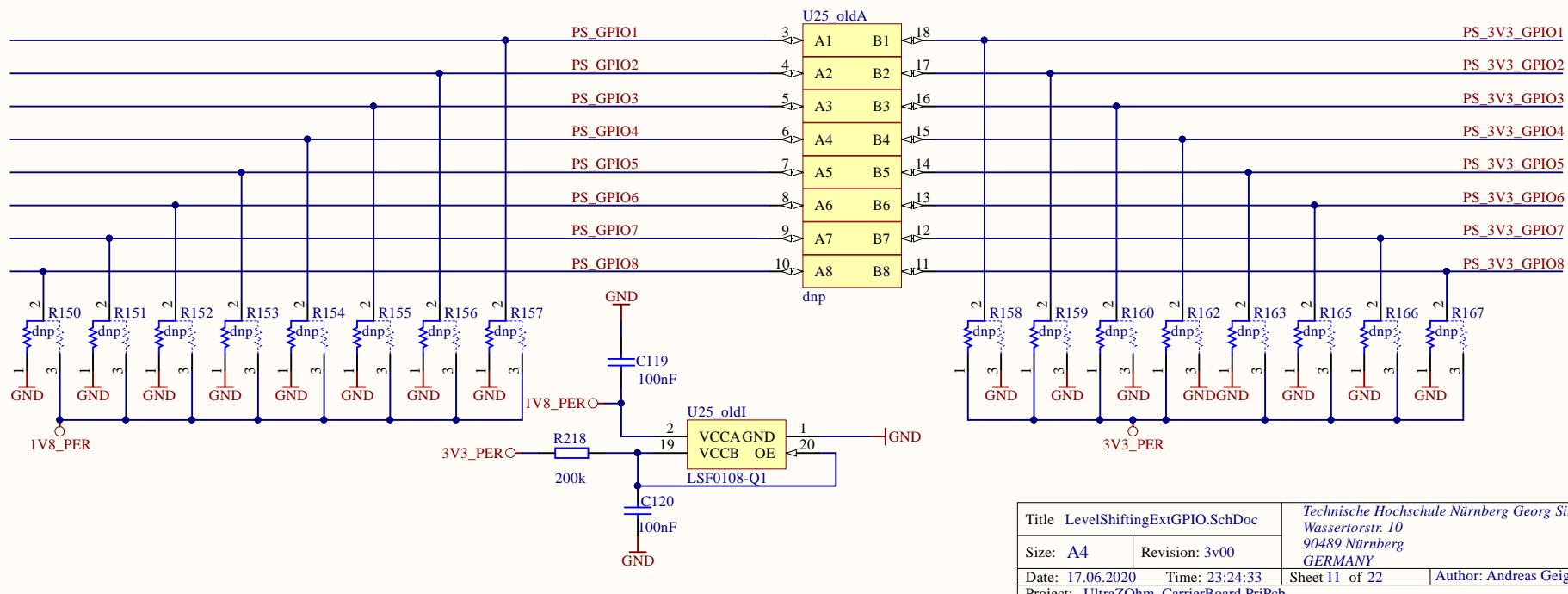


Note: In the layout
U25_old and U25_new do
not have a alphabetical
suffix it is only called
U25_old and U25_new.

Either the old or the new
level shifter must be
assembled but not both


Title: LevelShiftingExtGPIO.SchDoc	Technische Hochschule Nürnberg Georg Simon Ohm Wassertorstr. 10 90489 Nürnberg GERMANY
Size: A4	Revision: 3v00
Date: 17.06.2020	Time: 23:24:33
Project: UltraZOHM_CarrierBoard.PnjPcb	Sheet 11 of 22 Author: Andreas Geiger




A

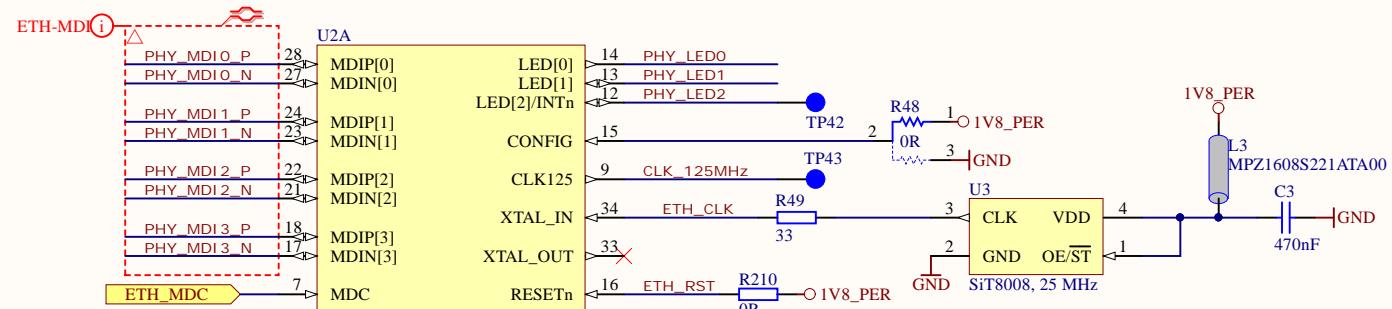



B

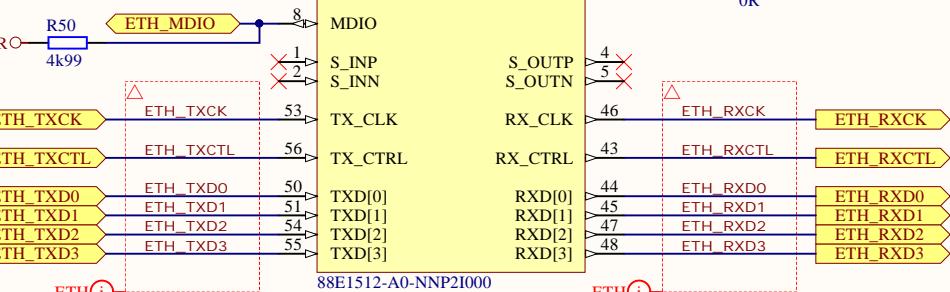

C

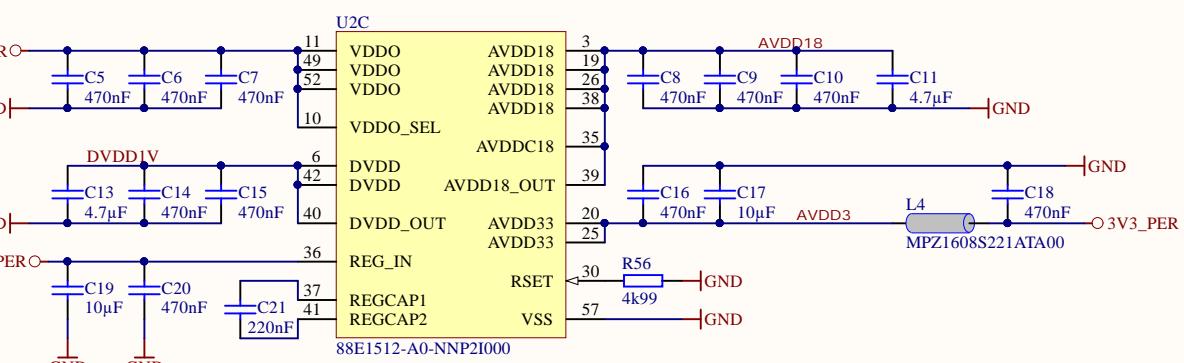


D

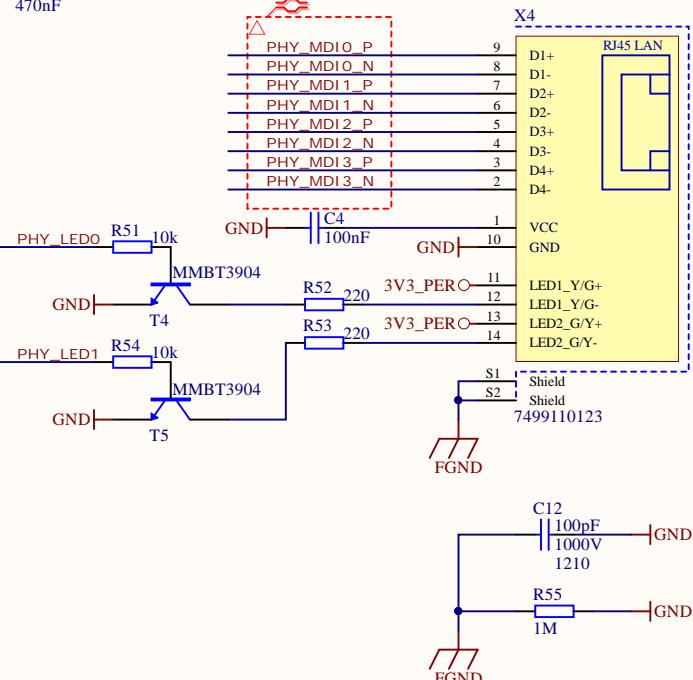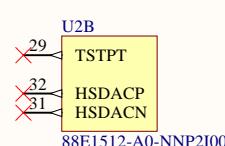




A

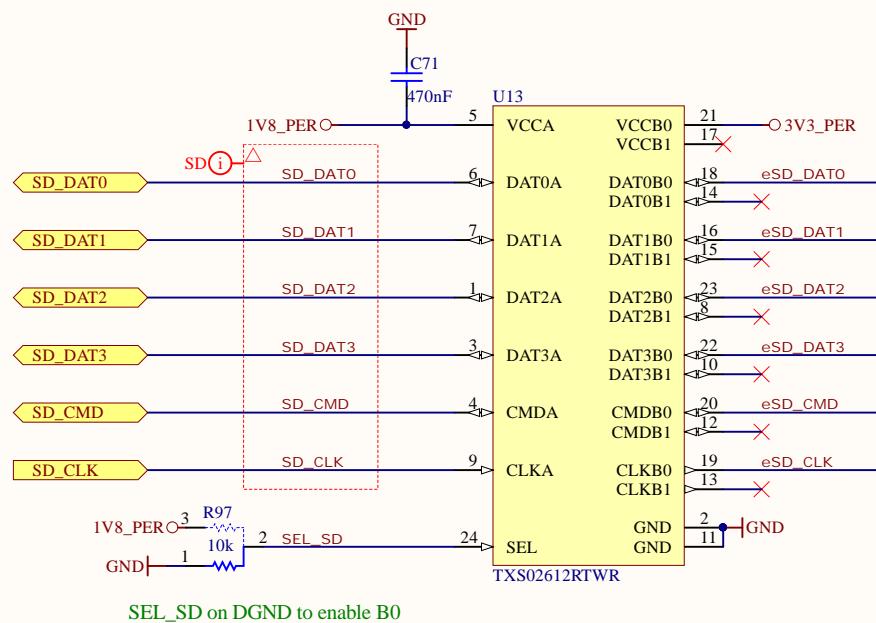Bidirectional Level Shifting 1.8V to 3.3V




SD Card Connector

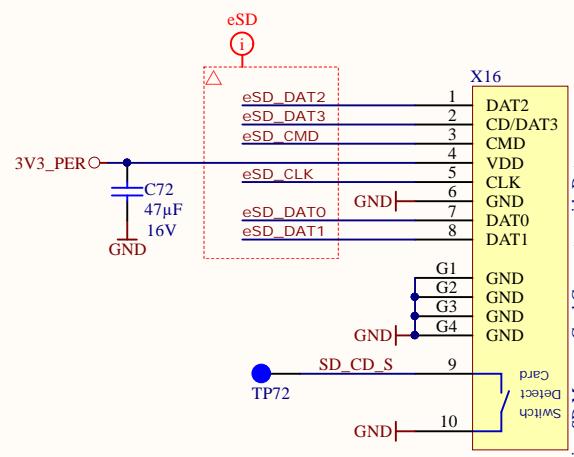



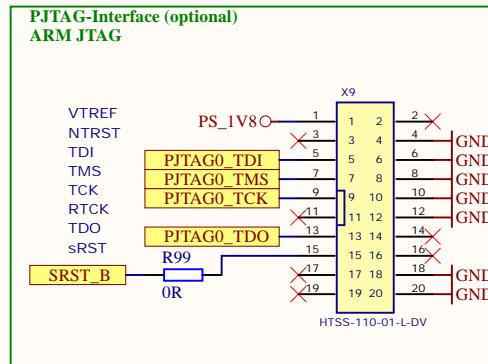
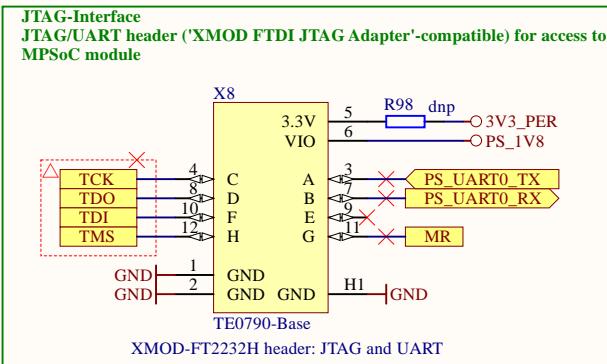


SPI, UART and I2C Connector @ 3.3V level

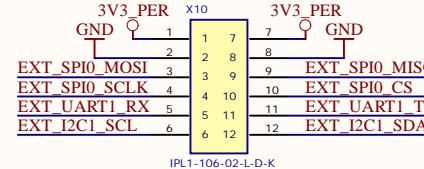

IPL1-106-02-L-D-K

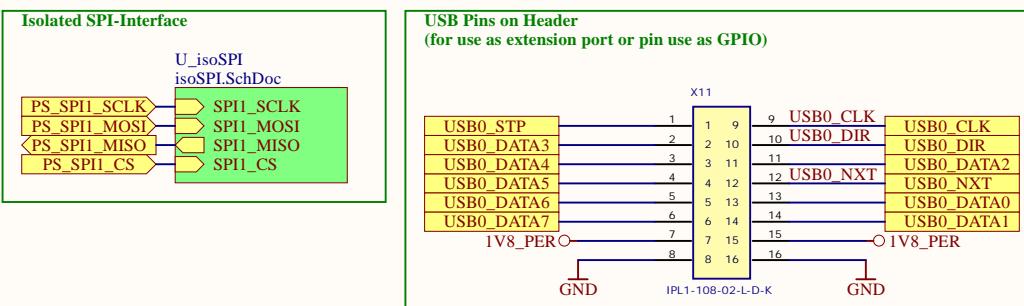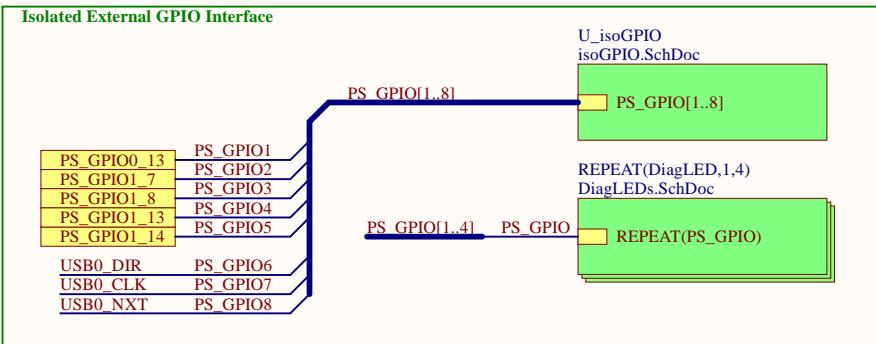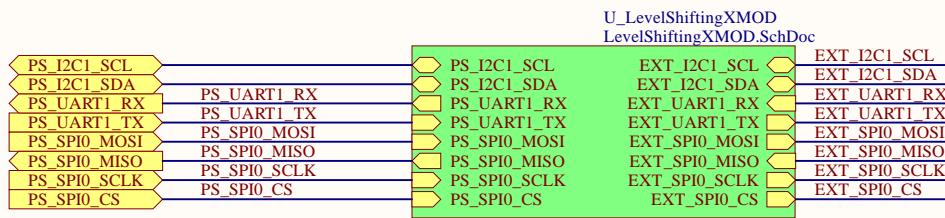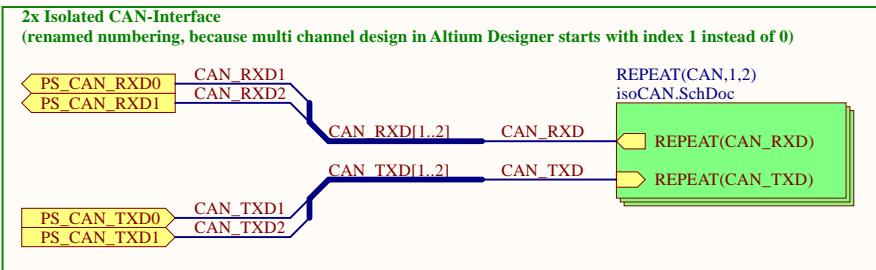Bidirectional Level Shifting 1.8V to 3.3V




Title XMOD.SchDoc		<i>Technische Hochschule Nürnberg Georg Simon Ohm Wassertorstr. 10 90489 Nürnberg GERMANY</i>		
Size: A4	Revision: 3v00			
Date: 17.06.2020	Time: 23:24:33	Sheet 14 of 22	Author: Andreas Geiger	
Project: UltraZOhm CarrierBoard.PriPcb				

A


LV side

Isolated side

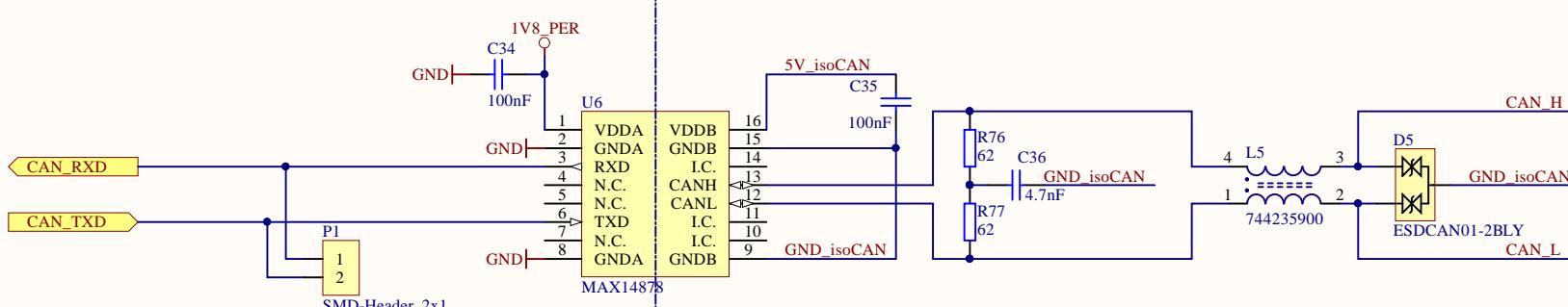


2pol Pin-Header for debugging purposes
(or do not place CAN PHY chip on-board
and use RXD and TXD externally)


CAN Connector

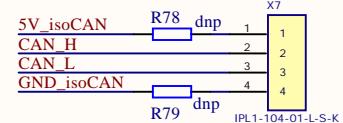


Isolated Power Supply

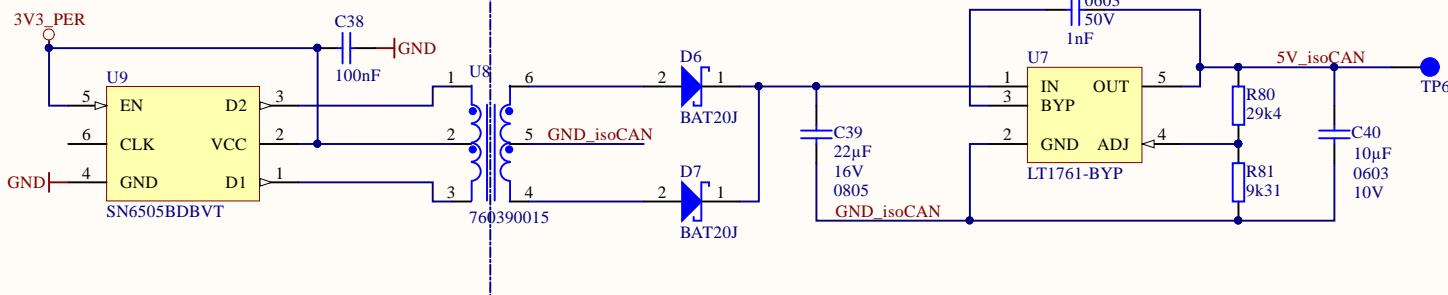


Level Shifting 1.8V to 3.3V

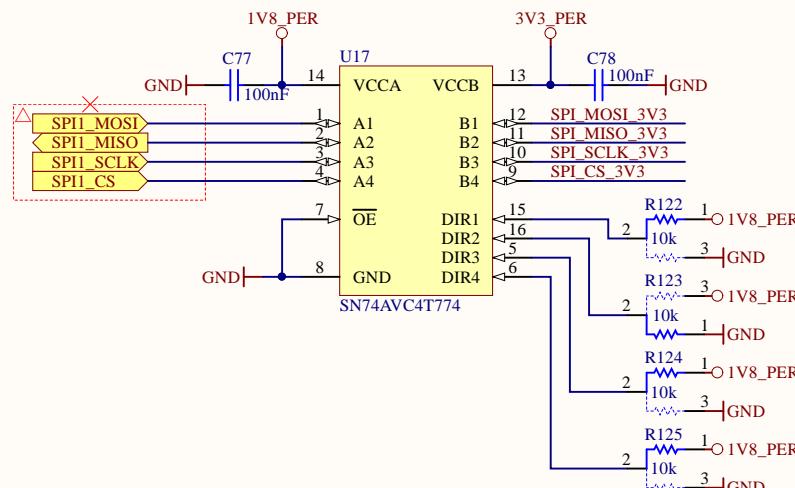


LV side

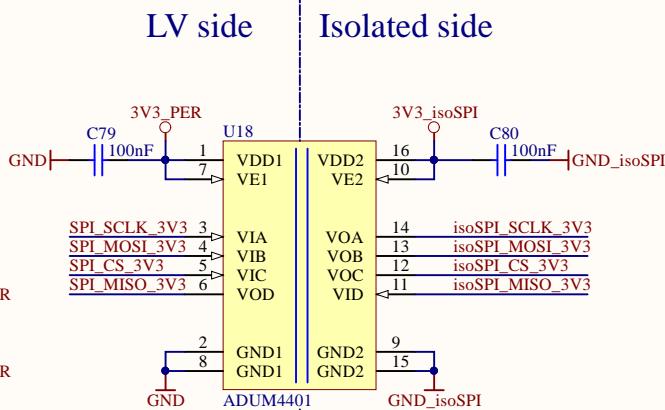

Isolated side

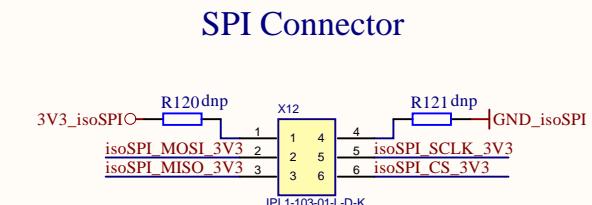

Isolated Power Supply

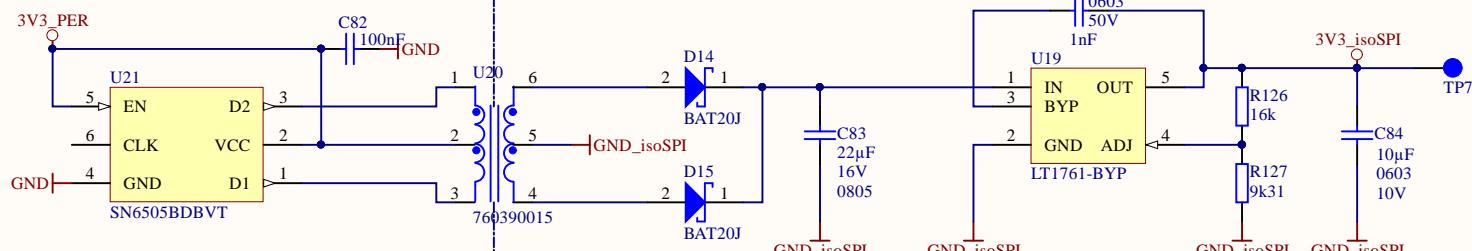

Bidirectional Level Shifting 1.8V to 3.3V

LV side



Isolated side

IO Protection with TVS-Diode and PTC-Resistor

A

A

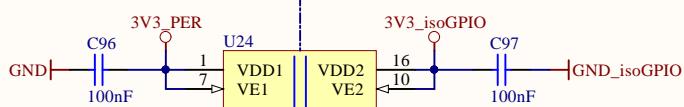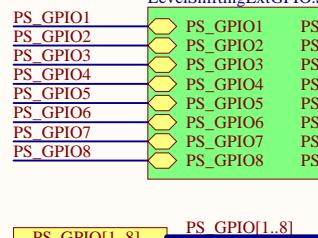
U_LevelShiftingExtGPIO
LevelShiftingExtGPIO.SchDoc



PS_GPIO1 PS_3V3_GPIO1
PS_GPIO2 PS_3V3_GPIO2
PS_GPIO3 PS_3V3_GPIO3
PS_GPIO4 PS_3V3_GPIO4
PS_GPIO5 PS_3V3_GPIO5
PS_GPIO6 PS_3V3_GPIO6
PS_GPIO7 PS_3V3_GPIO7
PS_GPIO8 PS_3V3_GPIO8

PS_GPIO[1..8]

PS_GPIO[1..8]

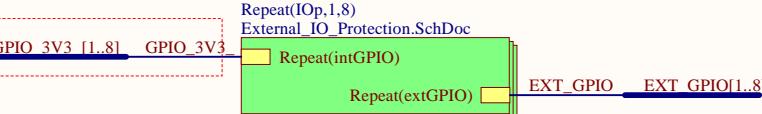

3V3_isoGPIO

GND_isoGPIO

3V3_iso

A

A

B

B


C

C


D

D

Voltage Divider

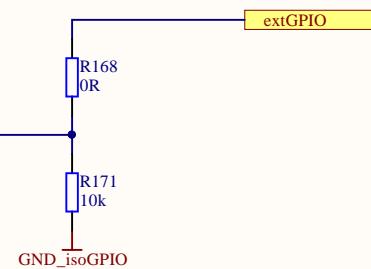

PTC for Overcurrent Protection

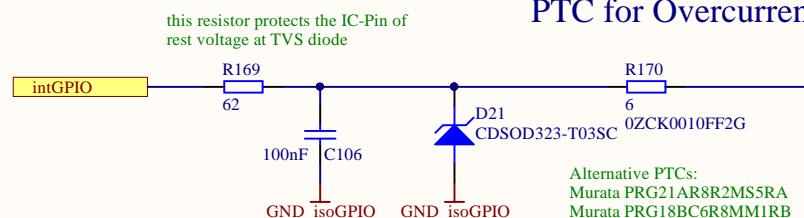

Title External_IO_Protection.SchDoc		Technische Hochschule Nürnberg Georg Simon Ohm Wassertorstr. 10 90489 Nürnberg GERMANY	
Size: A4	Revision: 3v00		
Date: 17.06.2020	Time: 23:24:34	Sheet 18 of 22	Author: Andreas Geiger
Project: UltraZOhm_CarrierBoard.PnjPcb			

A

A

B


B

C

C

D

D

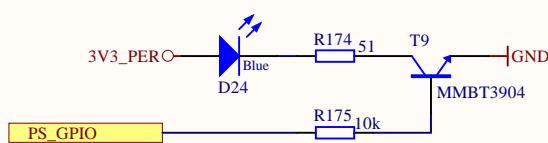


Title: DiagLEDs.SchDoc		Technische Hochschule Nürnberg Georg Simon Ohm Wassertorstr. 10 90489 Nürnberg GERMANY	
Size: A4		Revision: 3v00	
Date: 17.06.2020	Time: 23:24:34	Sheet 19 of 22	
Project: UltraZOhm_CarrierBoard.PnjPcb		Author: Andreas Geiger	

Notes: preferred to use 2x 22µF/50V capacitors at Vin, but this design uses 35V caps due to worse availability at distributors.

Datasheet: recommended minimum input capacitance is 22µF (including derating) ceramic with voltage rating

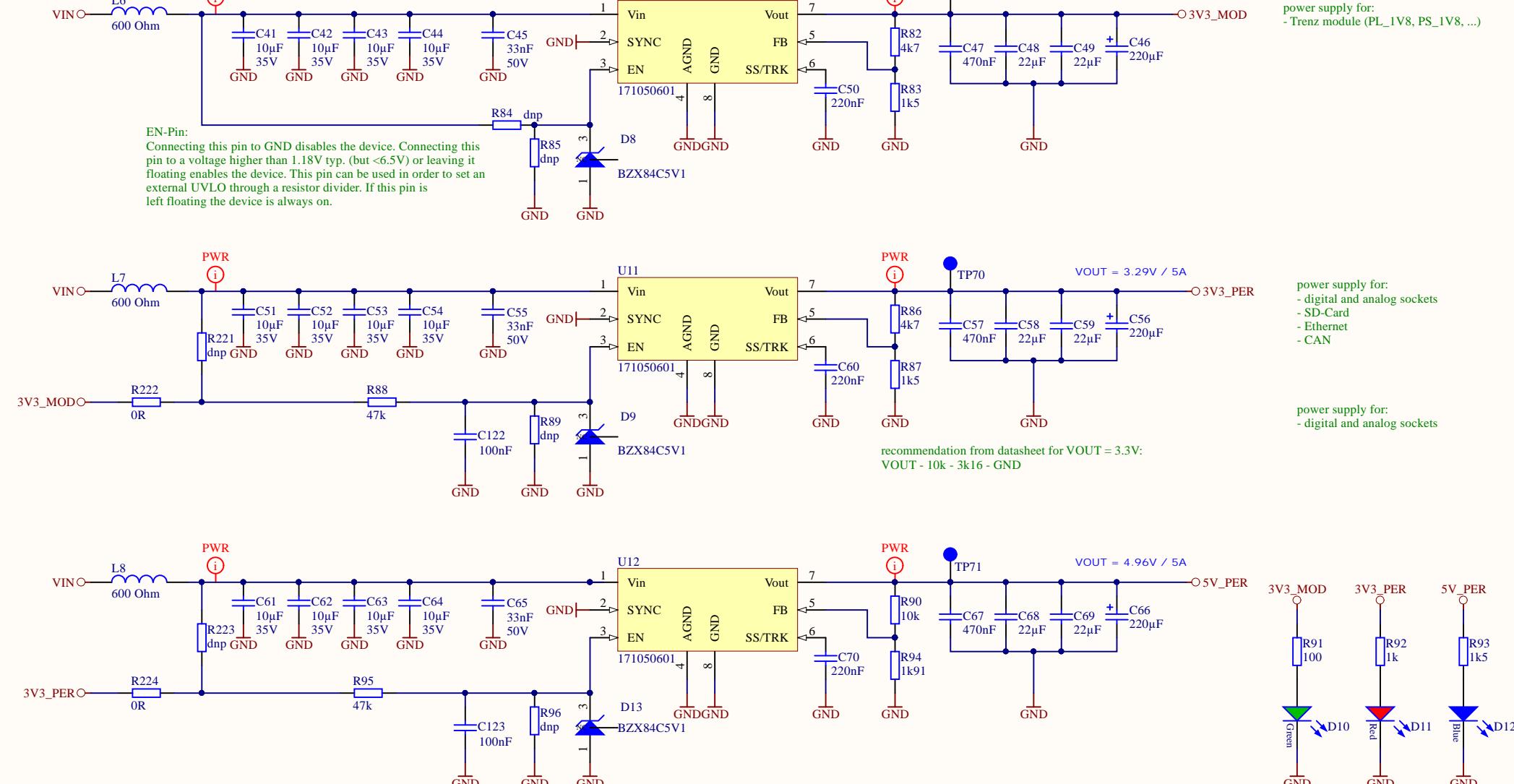at least 25% higher than the maximum applied input voltage for the application.



Title: Power_Supply_1.SchDoc	Technische Hochschule Nürnberg Georg Simon Ohm Wassertorstr. 10 90489 Nürnberg GERMANY	
Size: A4	Revision: 3v00	
Date: 17.06.2020	Time: 23:24:34	Sheet 20 of 22
Project: UltraZOHM_CarrierBoard.PnjPcb	Author: Andreas Geiger	

A

PG_Module

power good signal from Trenz module
to enable banks and peripherals after
module is supplied sufficiently

B

C


D

A

B

C


D

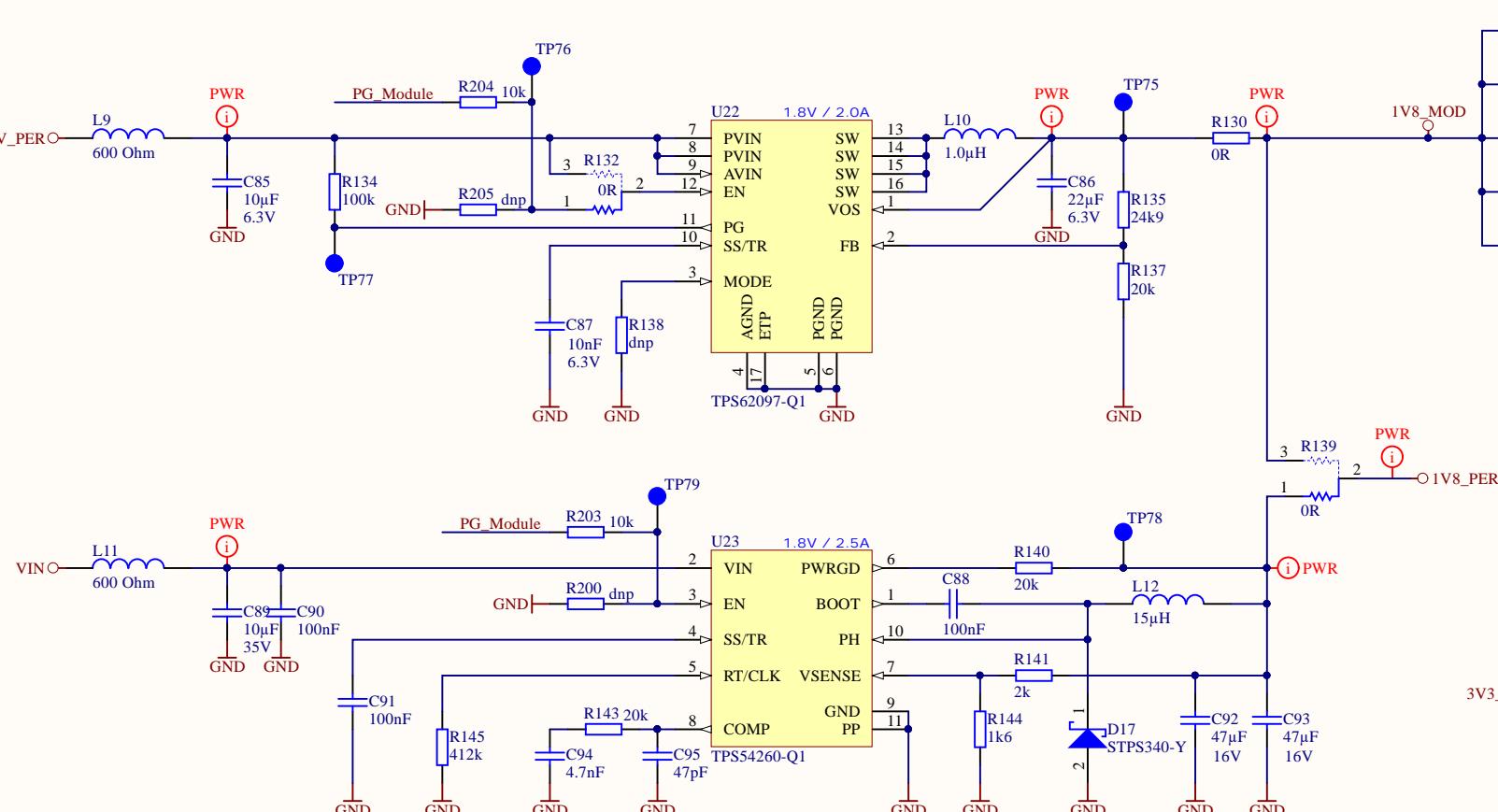


Reference Design: TE0728

Reference Design: TPS82085SIL (TE0808/POWER.SchDoc) not in stock at distributors...

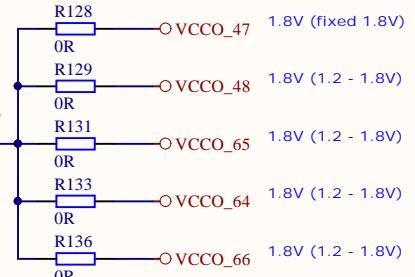bank power supply with jumper selectable
(place near to Trenz module!)



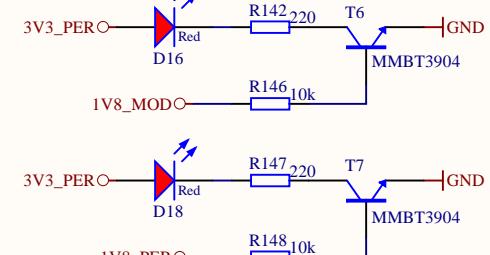power supply for:
 - CPLD Banks
 - I2C Level Shifter
 - Ethernet
 - SD-Card Level Shifter
 - JTAG Programmer
 - CAN Transceiver
 - SPI, UART, I2C-Interface Level Shifter
 - Isolated SPI Level Shifter
 - Isolated GPIO Level Shifter



Title Power_Supply_2.SchDoc

Size: A4 Revision: 3v00

Technische Hochschule Nürnberg Georg Simon Ohm
Wassertorstr. 10
90489 Nürnberg
GERMANY

Date: 17.06.2020 Time: 23:24:34 Sheet 21 of 22 Author: Andreas Geiger

Project: UltraZOHM_CarrierBoard.PnjPcb



A

A

B

B


C


C

D




D

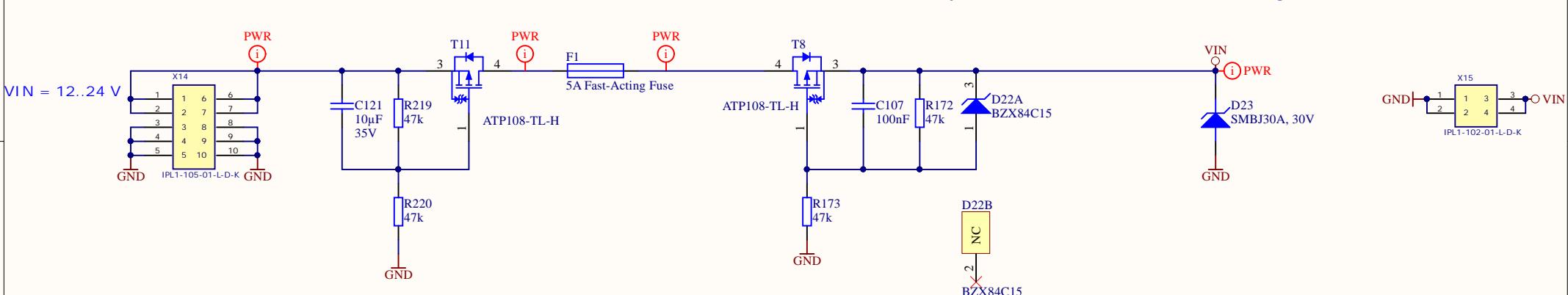Switch on current limitation Short Circuit Protection Reverse Polarity Protection Overvoltage Protection



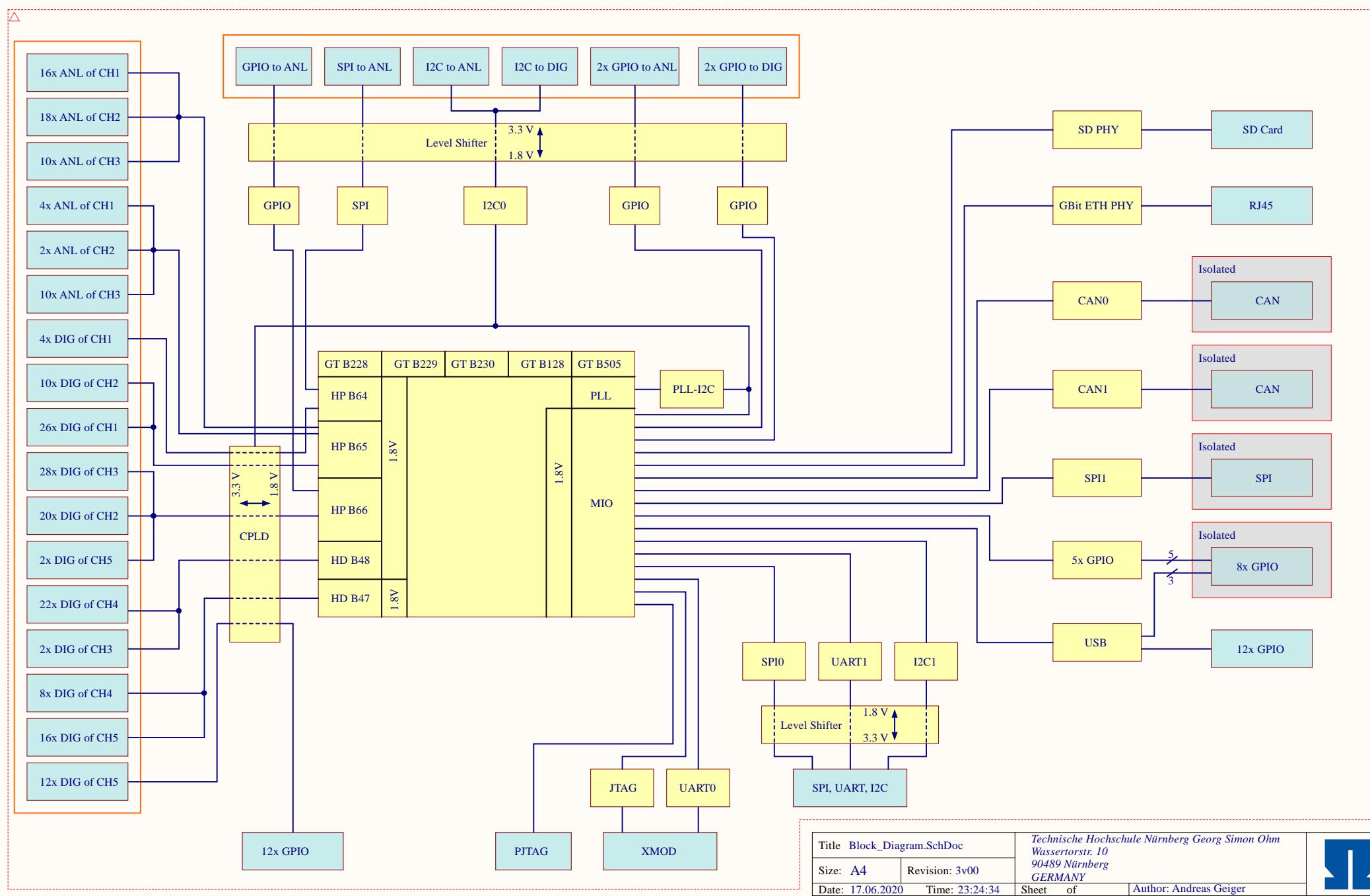

A

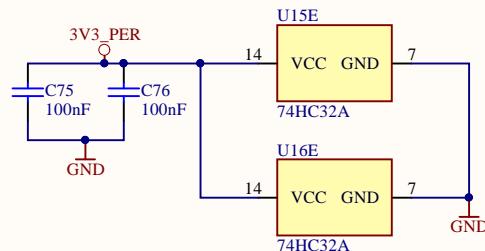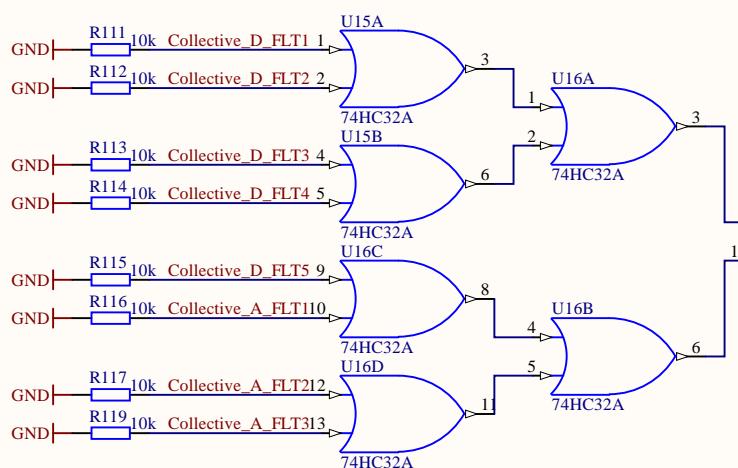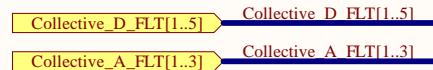

Note: The collective fault goes to the bidirectional level shifter that's why alium throws a warning (I/O against output)

testpoint for test purposes
to force a collective fault
error with an external 3.3V
probe

